

# CSIE 2344, Spring 2026: Laboratory 1

B13902022 Richard Lai

May 5, 2026

## 1 Source Code

### 1.1

---

```
1 module rca_g1(  
2     output C3,          // carry output  
3     output[2:0] S,      // sum  
4     input[2:0] A, B,    // operands  
5     input C0            // carry input  
6 );  
7  
8     wire c1, c2;  
9     FA fa0(c1, S[0], A[0], B[0], C0);  
10    FA fa1(c2, S[1], A[1], B[1], c1);  
11    FA fa2(C3, S[2], A[2], B[2], c2);  
12  
13 endmodule
```

---

### 1.2

---


```
1 module cla_g1(  
2     output C3,          // carry output  
3     output[2:0] S,      // sum  
4     input[2:0] A, B,    // operands  
5     input C0            // carry input  
6 );  
7  
8     wire [2:0] g, p, p_xor;  
9     wire c1, c2;  
10  
11    AND g_and0(g[0], A[0], B[0]);  
12    AND g_and1(g[1], A[1], B[1]);
```

```

13     AND g_and2(g[2], A[2], B[2]);
14
15     OR p_or0(p[0], A[0], B[0]);
16     OR p_or1(p[1], A[1], B[1]);
17     OR p_or2(p[2], A[2], B[2]);
18
19     XOR p_xor0(p_xor[0], A[0], B[0]);
20     XOR p_xor1(p_xor[1], A[1], B[1]);
21     XOR p_xor2(p_xor[2], A[2], B[2]);
22
23     wire p0c0;
24     AND and_p0c0(p0c0, p[0], C0);
25     OR or_c1(c1, g[0], p0c0);
26
27     wire g0p1, c0p0p1, c2_tmp;
28     AND and_c0p0p1(c0p0p1, p[1], p0c0);
29     AND and_g0p1(g0p1, g[0], p[1]);
30     OR or_c2tmp(c2_tmp, g[1], g0p1);
31     OR or_c2(c2, c2_tmp, c0p0p1);
32
33     wire g1p2, g0p1p2, c0p0p1p2;
34     AND4 and4_c0p0p1p2(c0p0p1p2, C0, p[0], p[1], p[2]);
35     AND and_g0p1p2(g0p1p2, g0p1, p[2]);
36     AND and_g1p2(g1p2, g[1], p[2]);
37
38     OR4 or4_c3(C3, g[2], g1p2, g0p1p2, c0p0p1p2);
39
40     XOR xor_s0(S[0], p_xor[0], C0);
41     XOR xor_s1(S[1], p_xor[1], c1);
42     XOR xor_s2(S[2], p_xor[2], c2);
43 endmodule

```

## 2 Waveform

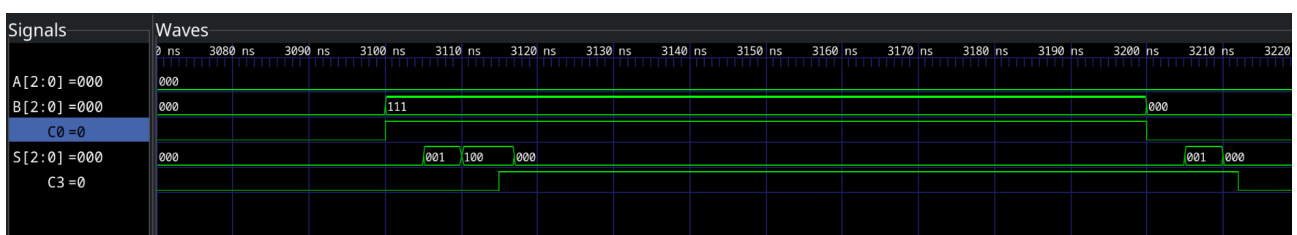

### 3 Propagation Delays

#### 3.1

The maximum delay is 23 ticks on transition  $000+000+0 \rightarrow 000+111+1$ .

#### 3.2

The maximum delay is 17 ticks on transition  $000+000+1 \rightarrow 000+000+0$ .